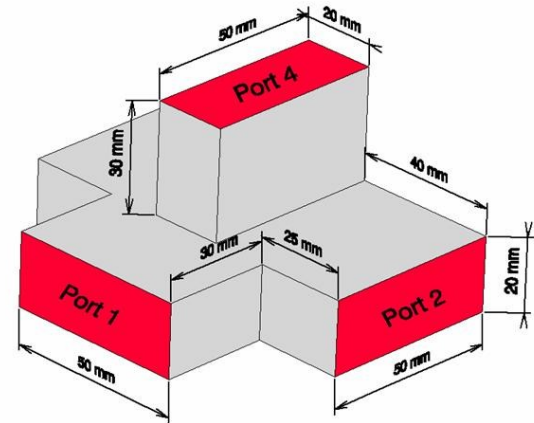


# PORTS

Y. Shlepnev  
Simberian Inc.

IBIS Interconnect Task Group Meeting  
December 11, 2024




# V, I, Waves and Multiport Descriptors

$\bar{V} = (V_1, V_2, \dots, V_N)^t$  - vector of port voltages

$\bar{I} = Y \cdot \bar{V}$  - admittance matrix

$\bar{I} = (I_1, I_2, \dots, I_N)^t$  - vector of port currents

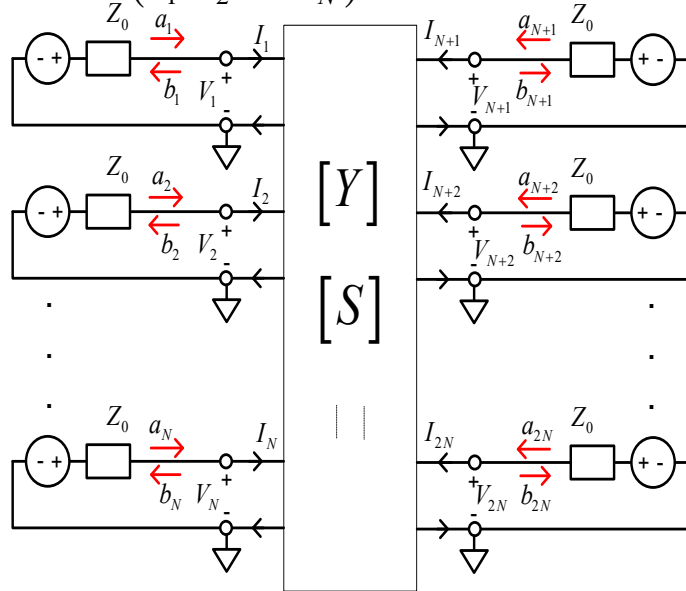$\bar{V} = Z \cdot \bar{I}$  - impedance matrix



$Z_0 = \text{diag}\{Z_{0i}, i = 1, \dots, N\} \in C^{N \times N}$  normalization impedances

$\bar{a} = \frac{1}{2} Z_0^{-1/2} \cdot (\bar{V} + Z_0 \cdot \bar{I})$  - vector of incoming waves

$\bar{b} = \frac{1}{2} Z_0^{-1/2} \cdot (\bar{V} - Z_0 \cdot \bar{I})$  - vector of outgoing waves

Scattering matrix (exists always):

$$\bar{b} = S \cdot \bar{a}, \quad S \in C^{N \times N}, \quad S_{i,j} = \left. \frac{b_i}{a_j} \right|_{a_k=0 \ k \neq j}$$

Potential of the reference terminals is unknown!

# Port Types


- Lumped ports – universal, but have limited bandwidth due to parasitic L and C (useful as low frequency approximation)

$$V = - \int_{ref}^{sig} \vec{E} \cdot d\vec{l} \quad I = \iint_S \vec{J}_p \cdot d\vec{s}$$

- Wave-ports or transmission line ports – preferable for decompositional analysis without frequency limits (deembedded)


$$V = \iint_S \vec{E} \times \vec{h} \cdot d\vec{s} \quad I = \iint_S \vec{e} \times \vec{H} \cdot d\vec{s}$$

VRP (common reference)

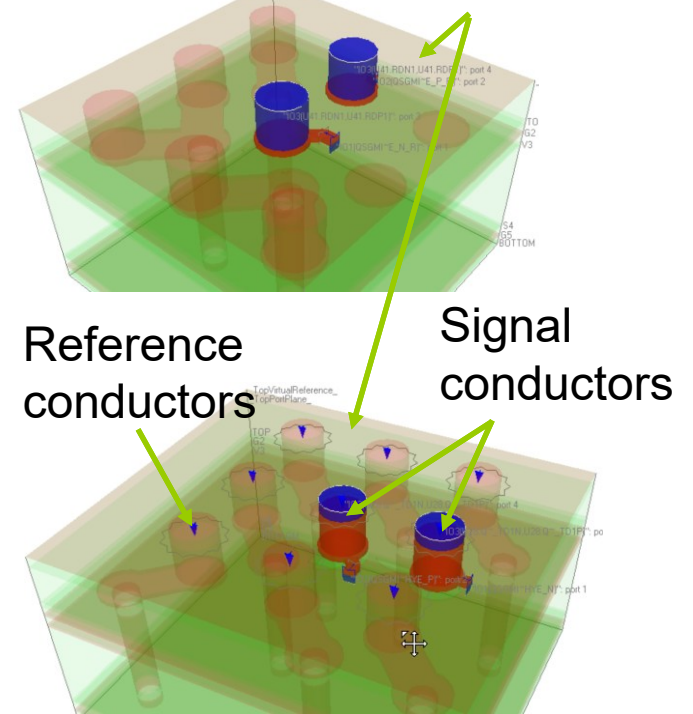

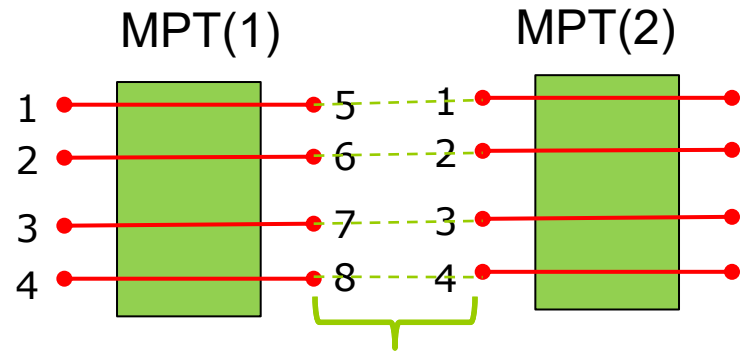
# Conditions and Operations

- Port is two terminals (signal and reference) with voltage (difference of potentials) and currents flowing in opposite direction (**cannot be cross-probed or cross-referenced**)
- Current to the signal terminal must be equal to the current from the reference terminal (**current equality condition**)
  - Only 2 ports can be connected together to preserve the current equality
- Connected ports must have exactly the same physical signal and reference conductors or geometry (**continuity condition**)




Connect port with identical definition (or at least same signal-reference conductors)

# Reference Conductor Disappearance

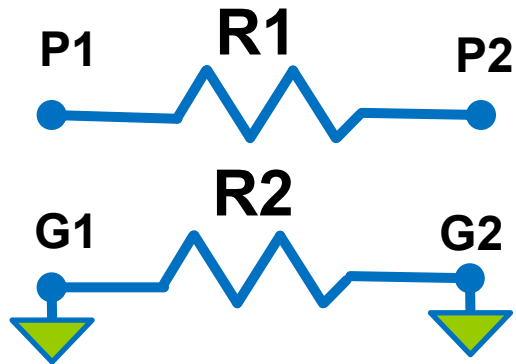


$$Y_{11}=Y_{22}=1/(R1+R2)$$
$$Y_{12}=Y_{21}=-1/(R1+R2)$$
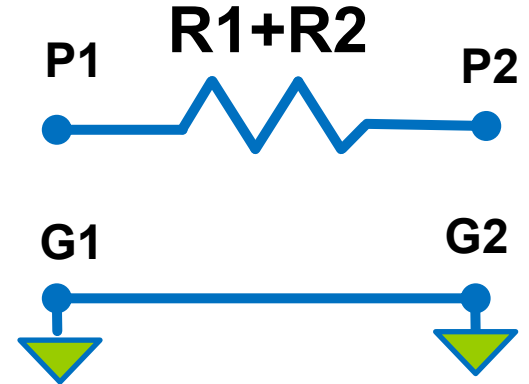
$$S_{11}=S_{22}=R1+R2/(R1+R2+2*Zo)$$
$$S_{12}=S_{21}=2*Zo/(R1+R2+2*Zo)$$



- Information about what is in the signal path and what is in the reference path is lost!
  - There is no way to separate R1 and R2 from sum in Y or S parameters;
- Association of the local reference with the global one will not neglect the information about ground resistance R2;
  - The relative port voltages and currents will be correct, though, there is no way to recover potential difference (voltage) between G1 and G2 and between P1 and P2;

# Separate Reference Conductor (Virtual)

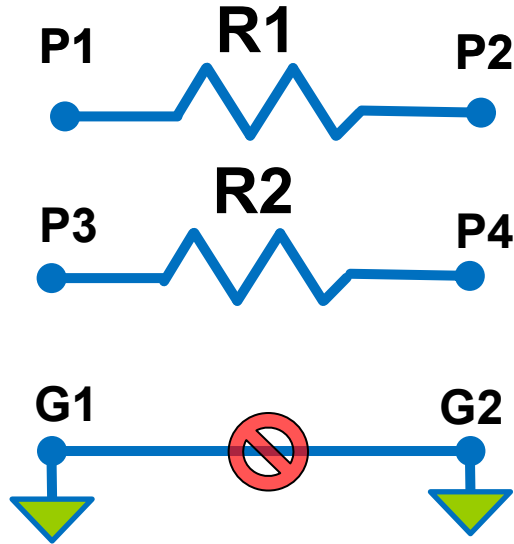

$$Y_{11}=Y_{22}=1/R_1$$
$$Y_{12}=Y_{21}=-1/R_1$$
$$Y_{33}=Y_{44}=1/R_2$$
$$Y_{34}=Y_{43}=-1/R_2$$


$$S_{11}=S_{22}=\mathbf{R1}/(\mathbf{R1}+2*Z_0)$$
$$S_{12}=S_{21}=2*Z_0/(\mathbf{R1}+2*Z_0)$$
$$S_{33}=S_{44}=\mathbf{R2}/(\mathbf{R2}+2*Z_0)$$
$$S_{34}=S_{43}=2*Z_0/(\mathbf{R2}+2*Z_0)$$

**Not usable if it is not real**


Can be always done in circuit domain, **but not in EM analysis**

Transmission lines: N+1 conductors - **+1 conductor should be natural**

# Un-Connected Reference Conductors

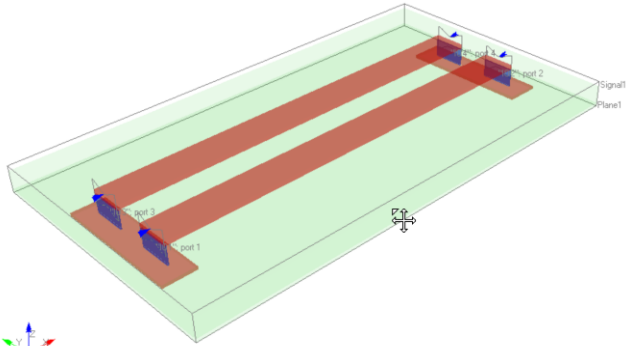


Why ~6 dB? →

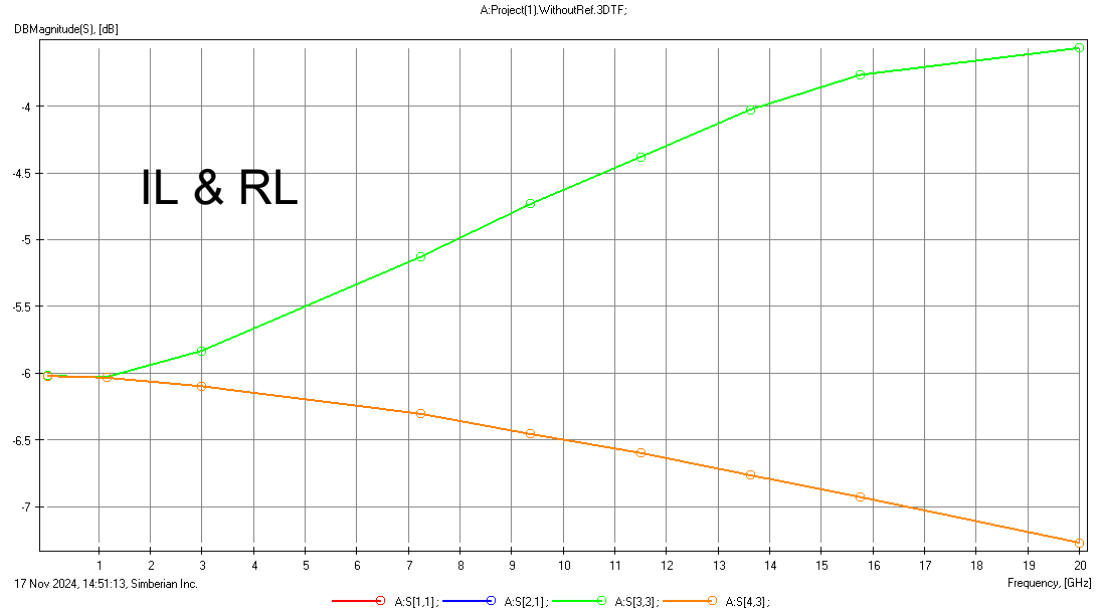

# Reference

Return current through  $2 \cdot Z_0$

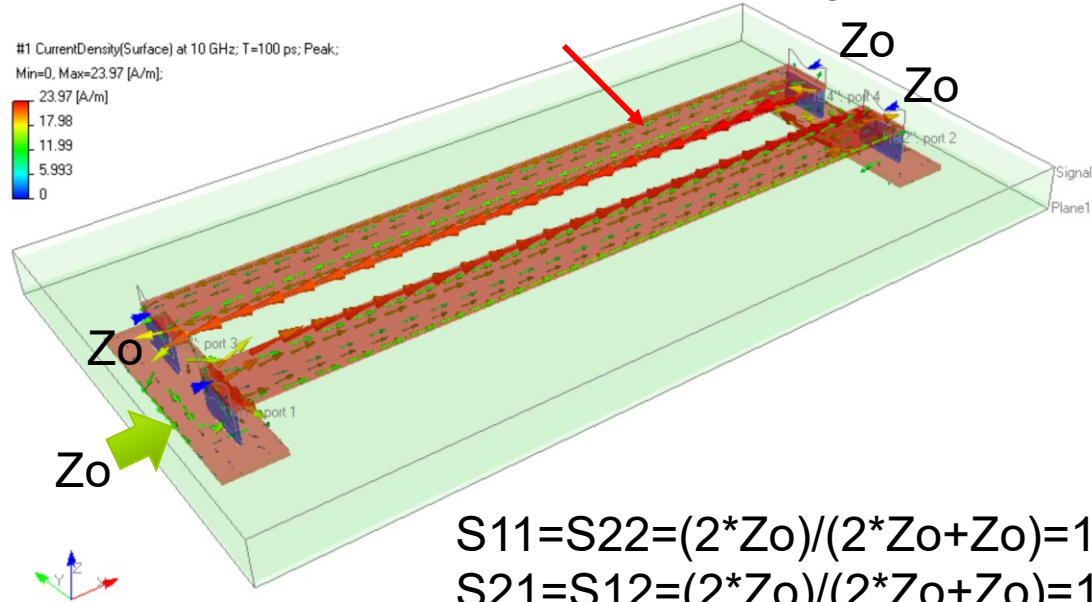


$$S_{11}=S_{22}=(2 \cdot Z_0)/(2 \cdot Z_0+Z_0)=1/2 \text{ (-6dB)}$$


$$S_{21}=S_{12}=(2 \cdot Z_0)/(2 \cdot Z_0+Z_0)=1/2 \text{ (-6dB)}$$
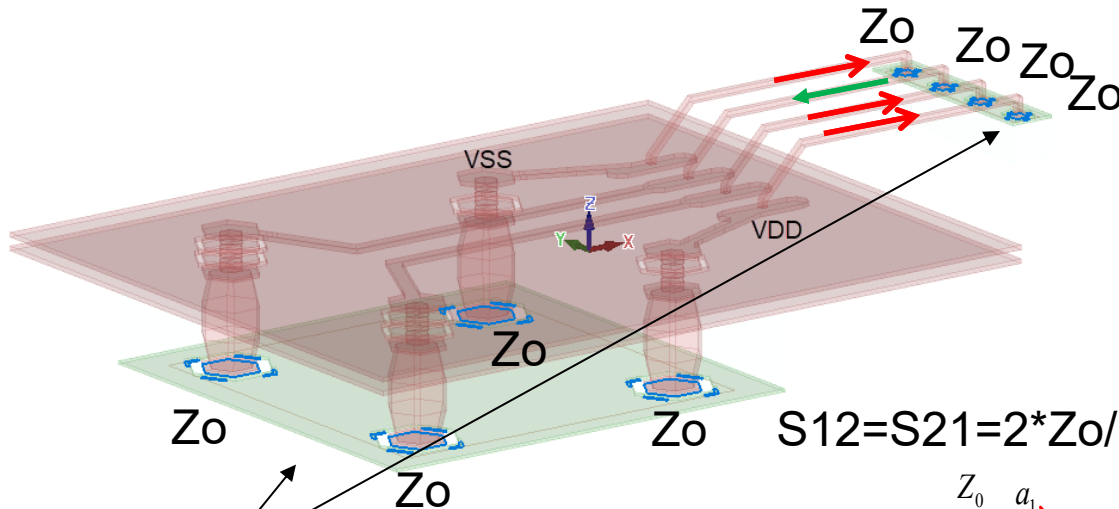
# Only Local References


From W. Beal, Floating Reference for S-Parameter Measurement



Virtual floating reference conductors

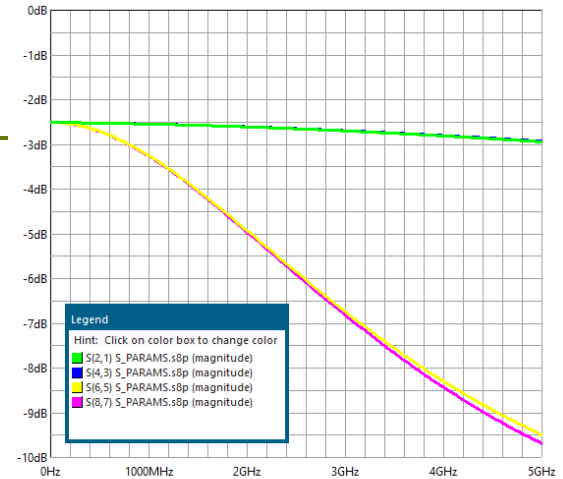

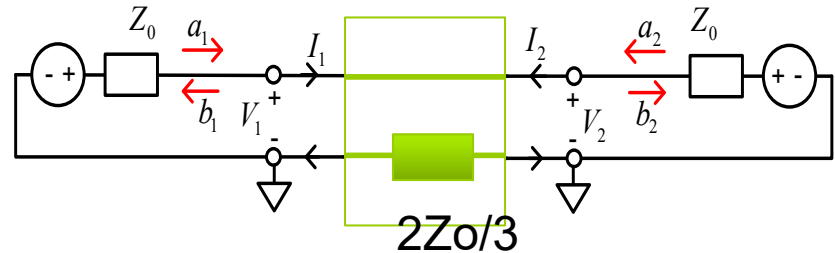
$$S_{12}=S_{21}=\frac{2 \cdot Z_0}{\left(\frac{2 Z_0}{3}+2 \cdot Z_0\right)}=0.75(-2.47 \text{ dB})$$



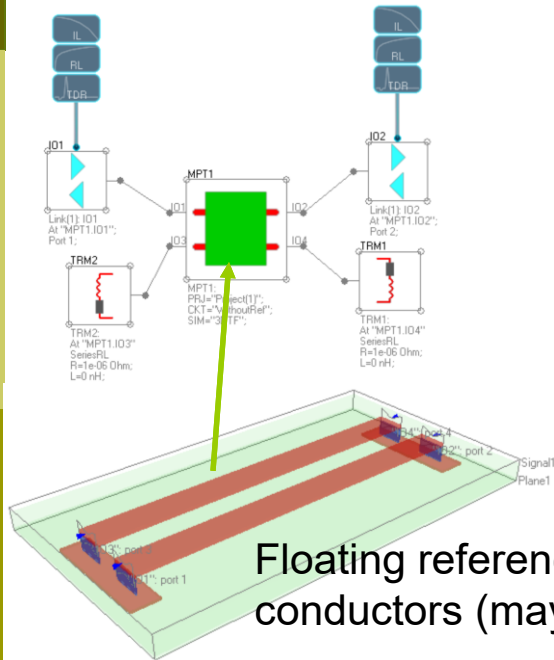
# Getting Common Reference


Establish common reference by shorting some ports



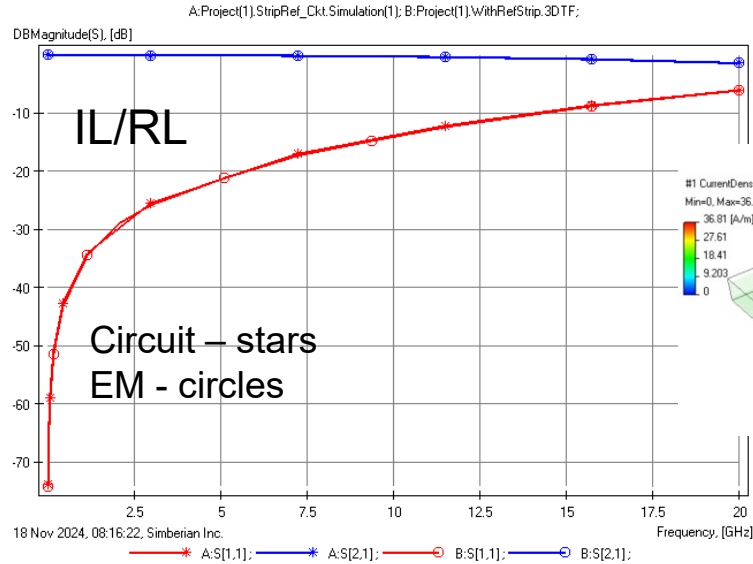Floating reference conductors (may be virtual)



Establish common reference in EM model

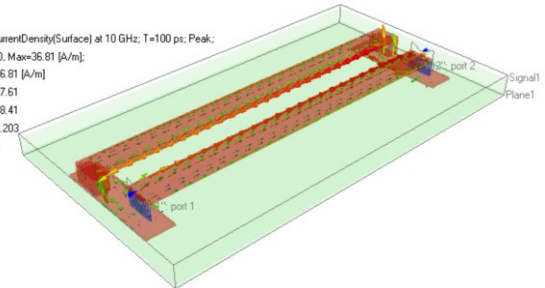

Natural reference conductor


# Virtual/Floating vs. Natural

---

- ❑ Virtual/floating reference is convenient to establish common reference for a group of ports
- ❑ There are always parasitics associated with that
- ❑ Virtual references can be used only at lower frequencies or if the effect is removed (deembedded)
- ❑ Natural referencing is always preferable choice (GND, VDD, VSS or all of them – depends on a particular case)
- ❑ All PDNs are natural references for transmission lines – interaction of signal nets with PDNs takes place only at transition points (change of reference conductors)


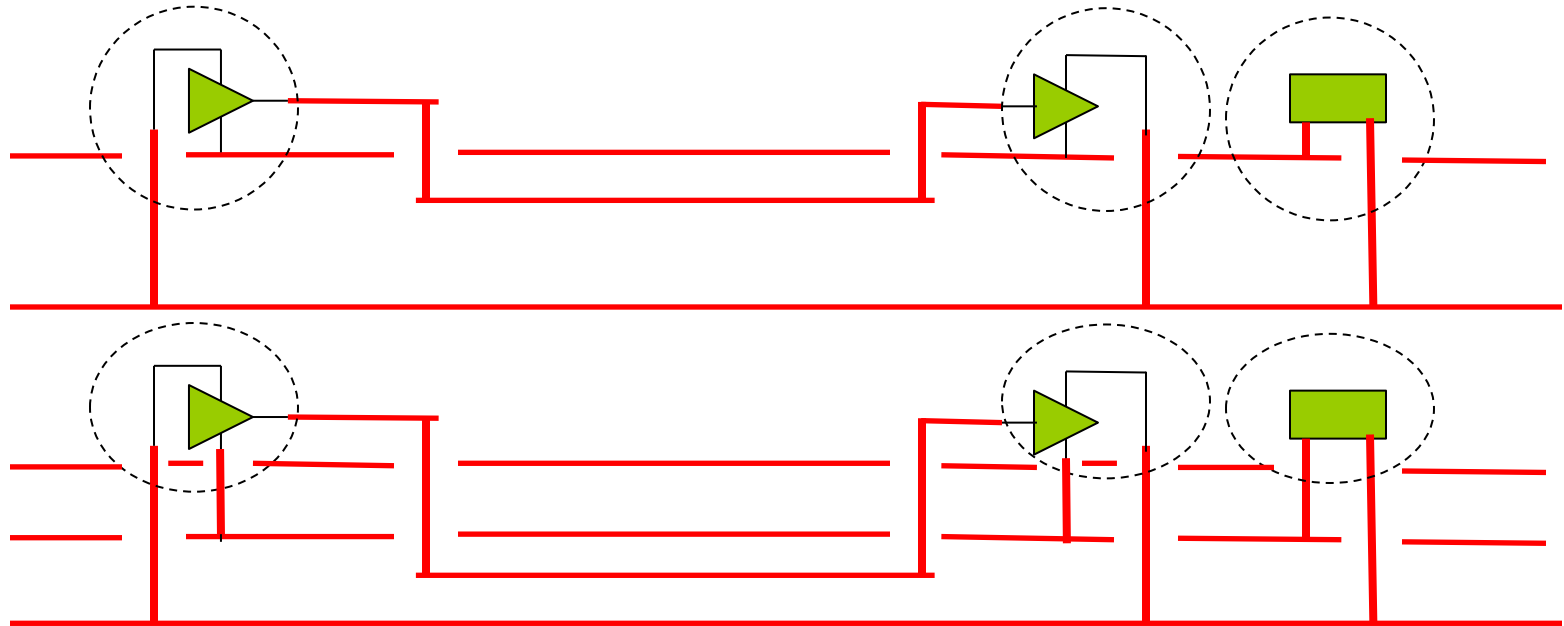
# Change of Reference in a Link

Same reference conductors should be used for ports to connect circuits





Distributed EM model should take care of the rest...

# Change of Reference in PDNs

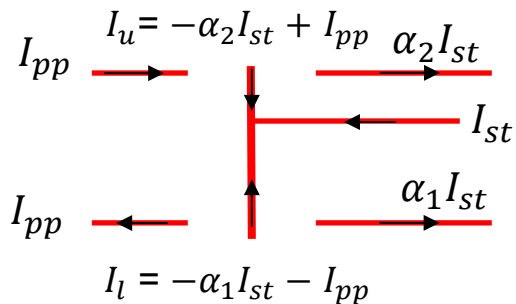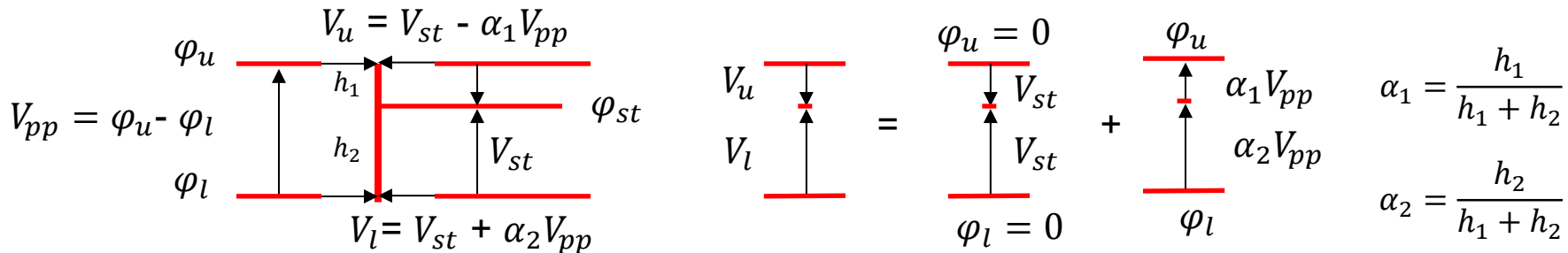


4-port circuit

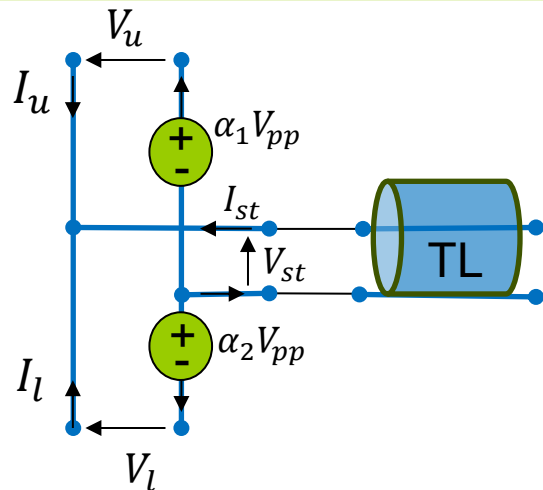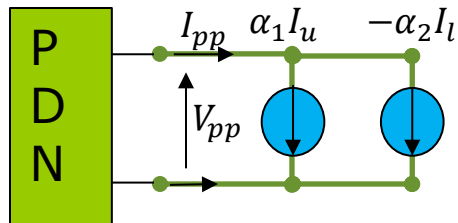


Y.O. Shlepnev, "Transmission plane models for parallel-plane power distribution system and signal integrity analysis", ACES'2006, 2006, p. 382-389.

# Change of Reference Junction

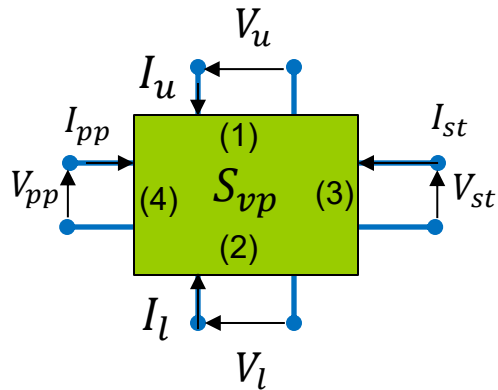


$$S_{vp} = \frac{1}{\beta} \begin{pmatrix} \alpha_1^2 - \alpha_2^2 & -2\alpha_1\alpha_2 + 2 & 2\alpha_2 + 2 & -2\alpha_1 - 2 \\ -2\alpha_1\alpha_2 + 2 & -\alpha_1^2 + \alpha_2^2 & 2\alpha_1 + 2 & 2\alpha_2 + 2 \\ 2\alpha_2 + 2 & 2\alpha_1 + 2 & \alpha_1^2 + \alpha_2^2 - 2 & 2\alpha_1 - 2\alpha_2 \\ -2\alpha_1 - 2 & 2\alpha_1 - 2\alpha_2 & 2\alpha_1 - 2\alpha_2 & 2 - \alpha_1^2 - \alpha_2^2 \end{pmatrix}$$

$$\beta = \alpha_1^2 + \alpha_2^2 + 4$$

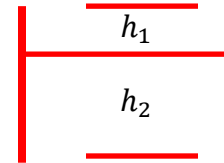

$$\alpha_1 = \frac{h_1}{h_1 + h_2}$$

$$\alpha_2 = \frac{h_2}{h_1 + h_2}$$

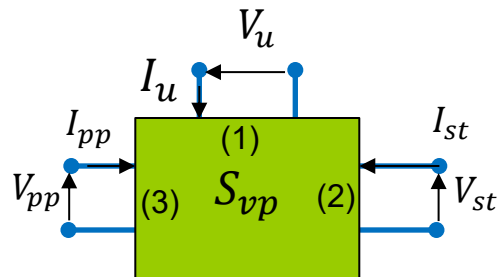

$$S_{vp} = \frac{1}{\gamma} \begin{pmatrix} \alpha_1^2 & 2 & -2\alpha_1 \\ 2 & \alpha_1^2 & 2\alpha_1 \\ -2\alpha_1 & 2\alpha_1 & 2 - \alpha_1^2 \end{pmatrix}$$

$$\gamma = \alpha_1^2 + 2$$

# Possible Touchstone Extensions

---

- Add information about ports physical structure
  - Lumped or wave-port (t-line port)
  - Reference conductors